

HOMework1

Source code

```
`timescale 1ns/1ns

module comb_logic(
    input a,b,c,
    output f
);
    wire n1,n2,n3;

    assign n1 = ~ a;
    assign n2 = n1 & b;
    assign n3 = a ^ c;
    assign f = n2 | n3;

endmodule
```

Testbench code



```
`timescale 1ns/1ns

module test;
    reg a,b,c;
    wire f;
    integer i;

    comb_logic uut(
        .a(a),
        .b(b),
        .c(c),
        .f(f)
    );

    always begin
        for(i=0;i<=7;i=i+1) begin
            {a,b,c}=i;
            #10;
        end
        $finish;
    end
endmodule
```

Simulation waveform

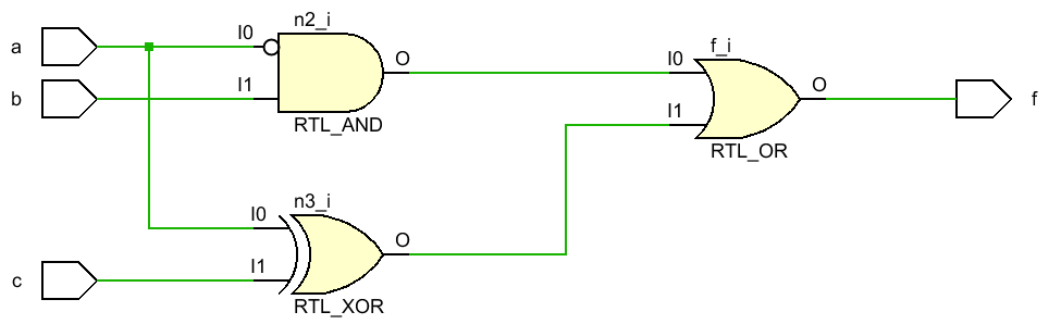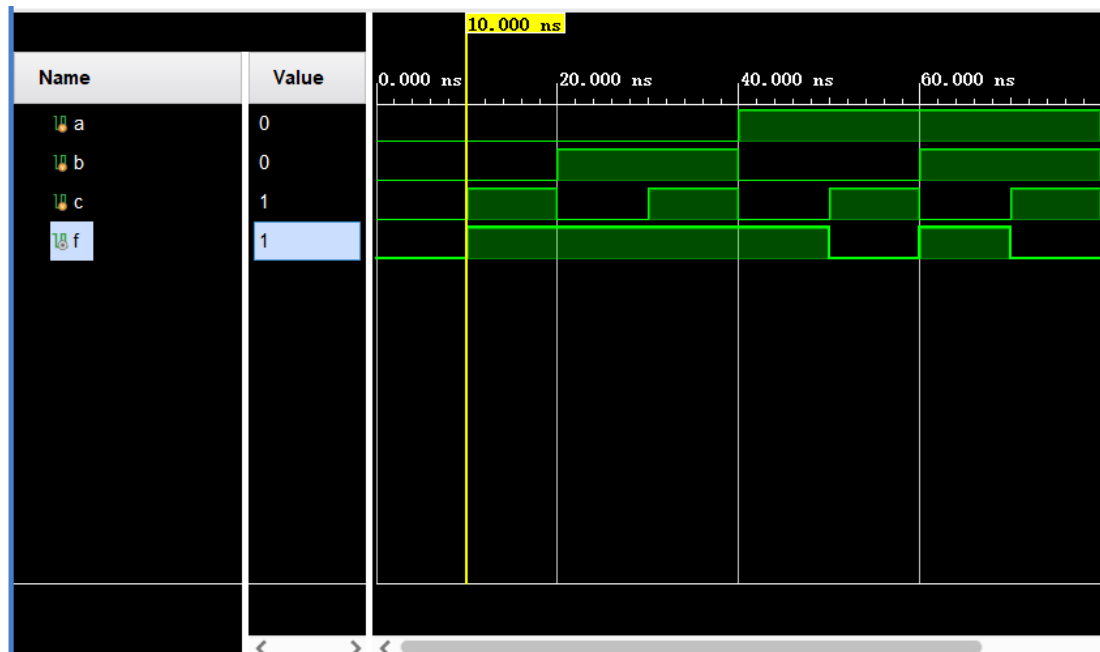

HOMEWORK2

Source code

```
`timescale 1ns/1ns

module odd_check #(
    parameter N=8
) (
    input [N-1:0] din,
    output dout
);

    assign dout=~(^din);

endmodule
```

Testbench code

```
`timescale 1ns/1ns

module test;

    reg [1:0] din_2;
    reg [3:0] din_4;
    reg [5:0] din_6;
    wire dout_2,dout_4,dout_6;

    odd_check #(
        .N(2)
    ) odd_check_2_inst (
        .din(din_2),
        .dout(dout_2)
    );

    odd_check #(
        .N(4)
    ) odd_check_4_inst (
        .din(din_4),
        .dout(dout_4)
    );

    odd_check #(
        .N(6)
    ) odd_check_6_inst (
        .din(din_6),
```

```

        .dout(dout_6)
    );

    integer force_i;
    initial begin
        for(force_i=0; force_i<2**6; force_i=force_i+1) begin
            din_2=force_i<2**2 ? force_i : 'bz;
            din_4=force_i<2**4 ? force_i : 'bz;
            din_6=force_i;
            #10;
        end
        $finish;
    end

    //check=1 :has odd '1' in total
    //check=0 :has even '1' in total
    wire check_2,check_4,check_6;
    assign check_2=(^din_2)^dout_2;
    assign check_4=(^din_4)^dout_4;
    assign check_6=(^din_6)^dout_6;

endmodule

```


Simulation waveform






有 2 位、4 位、6 位长的模版实例

testbench 的校验（不是设计的电路的校验位，那个是 dout）:

//check=1 :has odd '1' in total (din+dout)

//check=0 :has even '1' in total (din+dout)

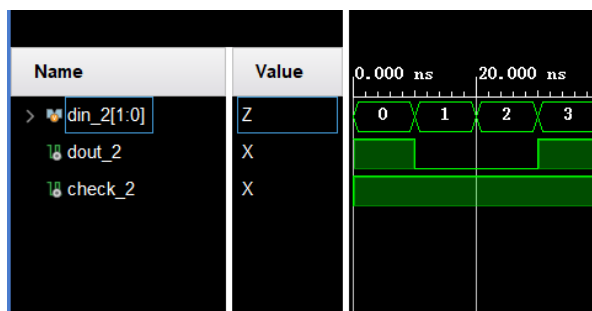

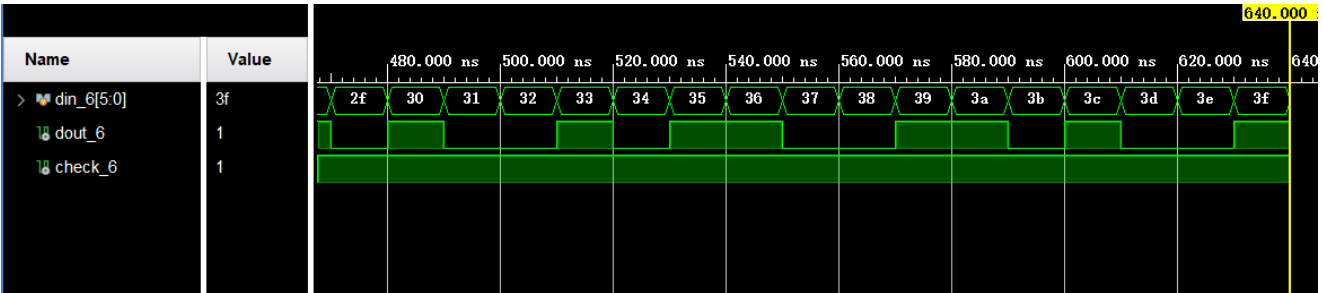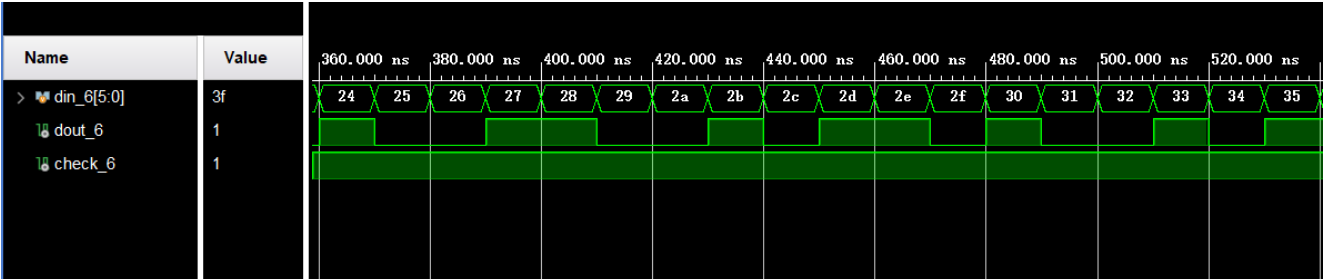 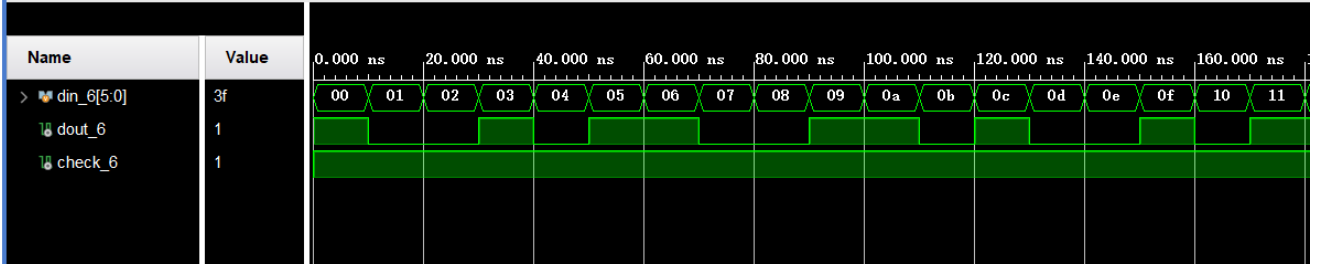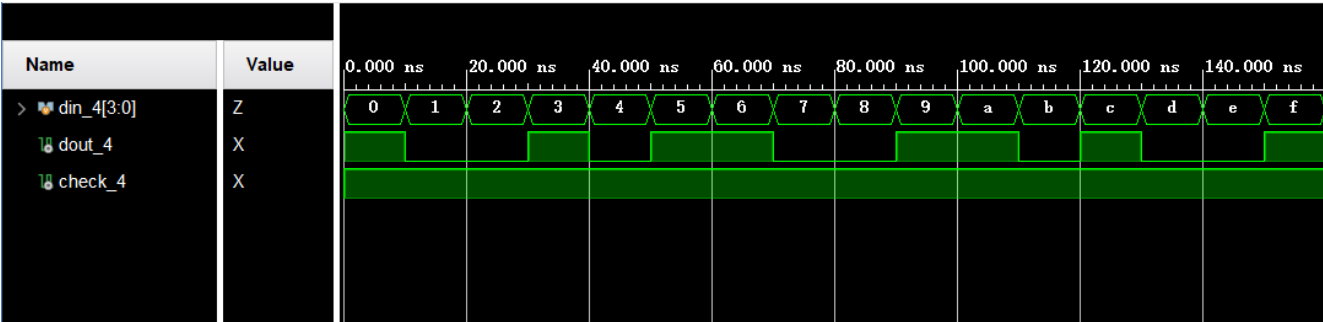

HOMework3

Source code

```
`timescale 1ns/1ns

module mux_4(
    input [3:0] din,
    input [1:0] sel,
    output reg dout
);

    always @(din,sel) begin
        case(sel)
            2'b00: dout=din[0];
            2'b01: dout=din[1];
            2'b10: dout=din[2];
            2'b11: dout=din[3];
            default: dout=1'bz;
        endcase
    end

    // assign dout=din[sel];

endmodule
```

Testbench code

```
`timescale 1ns/1ns

module test;
    wire [3:0] din;
    reg [1:0] sel;
    wire dout;

    mux_4 uut(
        .din(din),
        .sel(sel),
        .dout(dout)
    );

    assign din=4'bxz10;

    integer i;
    initial begin
        for(i=0;i<=3;i=i+1) begin
```


```

        sel=i;
        #10;
    end
    $finish;
end

endmodule

```

Simulation waveform

 

din 的[3:2]位有意设置 z 和 x。

HOMWORK4

Source code

```
`timescale 1ns/1ns

module comb_quality (
    input A,B,C,
    output reg F1,F2,F3
);

    always @(A,B,C) begin
        if(A && B && C)           //{A,B,C}=3'b111
            {F1,F2,F3}=3'b100;
        else if(A && (B || C))   //{A,B,C}=3'b101 || {A,B,C}=3'b110
            {F1,F2,F3}=3'b010;
        else if(~A && (B && C))  //{A,B,C}=3'b011
            {F1,F2,F3}=3'b001;
        else
            {F1,F2,F3}=3'b000;
    end

endmodule
```

Testbench code

```
`timescale 1ns/1ns

module test;
    reg A,B,C;
    wire F1,F2,F3;

    comb_quality uut(
        .A(A),
        .B(B),
        .C(C),
        .F1(F1),
        .F2(F2),
        .F3(F3)
    );

    integer i;
    initial begin
        for(i=0;i<=7;i=i+1) begin
            {A,B,C}=i[3:0];
            #10;
        end
    end
endmodule
```




```

        end
        $finish;
    end

endmodule

```

Simulation waveform

 

HOMEWORK5

Source code

```
`timescale 1ms/1ms

module counter_10 (
    input rst,
    input en,
    input clk1k,
    output reg [6:0] seg,
    output dig
);

    //clock division
    reg [7:0] cnt_clk;//0~249
    reg clk2hz;
    always @(posedge clk1k,posedge rst) begin
        if(rst) begin
            cnt_clk<=0;
            clk2hz<=0;
        end else if(en) begin
            if(cnt_clk==249) begin
                cnt_clk<=0;
                clk2hz <= ~clk2hz;
            end else
                cnt_clk<=cnt_clk+1;
        end
    end

    //count_10
    reg [3:0] cnt_num;//0~9
    always @(posedge clk2hz,posedge rst) begin
        if(rst)
            cnt_num<=0;
        else if(en) begin
            if(cnt_num==9)
                cnt_num<=0;
            else
                cnt_num<=cnt_num+1;
        end
    end

    //dig output
    always @(*) begin
        case(cnt_num)
```

```

        4'h0 : seg = 7'h3f;
        4'h1 : seg = 7'h06;
        4'h2 : seg = 7'h5b;
        4'h3 : seg = 7'h4f;
        4'h4 : seg = 7'h66;
        4'h5 : seg = 7'h6d;
        4'h6 : seg = 7'h7d;
        4'h7 : seg = 7'h07;
        4'h8 : seg = 7'h7f;
        4'h9 : seg = 7'h6f;
    endcase
end
assign dig=1'b0;

endmodule

```

Testbench code

```

`timescale 1ms/1ms

module test;

    reg rst;
    reg en;
    reg clk1k;
    wire [6:0] seg;
    wire dig;

    counter_10 count_10(
        .rst(rst),
        .en(en),
        .clk1k(clk1k),
        .seg(seg),
        .dig(dig)
    );

    //clk1k generate
    initial begin
        clk1k=0;
        #10;
        forever begin
            clk1k = ~clk1k;
            #1;
        end
    end

```

```

end


//rst and en
initial begin
    rst=1; en=0;
    #5;
    rst=0; en=1;
    #2000;
    rst=0; en=0;
    #4000;
    rst=1; en=0;
    #1000;
    rst=0; en=0;
    #3000;
    rst=0; en=1;
end

//finish time
always begin
    #500;
    if($time>=500*40)
        $finish;
end

endmodule

```

Simulation waveform

 

有下板测试

从右向左是复位、使能键。

HOMEWORK6

Source code

```
`timescale 1ms/1us

module water_led (
    input clk1MHz,
    input rst,
    output reg [7:0] led
);

    //clk division
    reg [18:0] cnt_clk;//0~500K
    reg clk1Hz;
    always @(posedge clk1MHz,posedge rst) begin
        if(rst) begin
            cnt_clk<=0;
            clk1Hz<=0;
        end else begin
            if(cnt_clk==500_000-1) begin
                cnt_clk<=0;
                clk1Hz <= ~clk1Hz;
            end else
                cnt_clk<=cnt_clk+1;
        end
    end

    //water led
    always @(posedge clk1Hz,posedge rst) begin
        if(rst)
            led<=8'b0000_0001;
        else
            led<={led[6:0],led[7]};
    end

endmodule
```

Testbench code

```
`timescale 1ms/1us

module test;
    reg clk1MHz;
    reg rst;
    wire [7:0] led;
```

```

water_led water_led(
    .rst(rst),
    .clk1MHz(clk1MHz),
    .led(led)
);

//clk1MHz generate
initial begin
    clk1MHz=0;
    #10;
    forever begin
        clk1MHz = ~clk1MHz;
        #0.001;
    end
end


//rst generate
initial begin
    rst=1;
    #5;
    rst=0;
    #6000 rst=1;
    #2000 rst=0;
    #7000 rst=1;
    #4000 rst=0;
end

//finish time
always begin
    #1000;
    if($time>=1000*40)
        $finish;
end

endmodule

```

Simulation waveform

 

有下板测试

一个复位键

HOMEWORK7

Source code

Traffic_light.v

```
`timescale 1ms/100us

module traffic_light (
    input CLK1K,
    input nRST,
    output [6:0] seg,
    output [5:0] dig,
    output [7:0] led
);

    //clk division
    wire CLK1Hz;
    clock_division #(.DIVCLK_CNTMAX(499))
        light_clock(
            .clk_in(CLK1K),
            .rst_n(nRST),
            .divclk(CLK1Hz)
        );

    //led show
    wire [3:0] num_1,num_2,num_5,num_6;
    led_show led_show(
        .rst_n(nRST),
        .CLK1K(CLK1K),
        .num_1(num_1),
        .num_2(num_2),
        .num_3(4'hA),
        .num_4(4'hA),
        .num_5(num_5),
        .num_6(num_6),
        .dig(dig),
        .seg(seg)
    );

    //bcd convert
    reg [5:0] num_A,num_B;
    bin2bcd bin2bcd_A(
```



```

        .bin(num_A),
        .bcd_1(num_1),
        .bcd_2(num_2)
    );
    bin2bcd bin2bcd_B(
        .bin(num_B),
        .bcd_1(num_5),
        .bcd_2(num_6)
    );

    //traffic time counter
    reg [5:0] cnt_traf;//0~59
    always @(posedge CLK1Hz,negedge nRST) begin
        if(~nRST)
            cnt_traf<=59;
        else begin
            if(cnt_traf==0)
                cnt_traf<=59;
            else
                cnt_traf<=cnt_traf-1;
        end
    end

    //A path control(59~30:stop; 29~0:start)
    reg [2:0] led_A;
    always @(*) begin
        if(!nRST) begin
            led_A=3'b000;
            num_A=cnt_traf-30+1;    //as cnt_traf=59
        end else if(cnt_traf>=30) begin
            led_A=3'b100;    //red light
            num_A=cnt_traf-30+1;
        end else if(cnt_traf>=5) begin
            led_A=3'b001;    //green light
            num_A=cnt_traf-5+1;
        end else begin
            led_A=3'b010;    //yellow light
            num_A=cnt_traf+1;
        end
    end

    //B path control(59~30:start; 29~0:stop)
    reg [2:0] led_B;
    always @(*) begin

```

```

        if(!nRST) begin
            led_B=3'b000;
            num_B=cnt_traf+1;    //as cnt_traf=59
        end else if(cnt_traf<=29) begin
            led_B=3'b100;    //red light
            num_B=cnt_traf+1;
        end else if(cnt_traf<=34) begin
            led_B=3'b010;    //yellow light
            num_B=cnt_traf-30+1;
        end else begin
            led_B=3'b001;    //green light
            num_B=cnt_traf-35+1;
        end
    end
end

//led mapping
assign led[7:5]=led_B;
assign led[2:0]=led_A;
assign led[4:3]=2'b00;

endmodule

```

led_show.v

```

module led_show(
    input rst_n,
    input CLK1K,
    input [3:0] num_1,num_2,num_3,num_4,num_5,num_6,
    output reg [5:0] dig,
    output reg [6:0] seg
);

//dig generate
always @(posedge CLK1K,negedge rst_n) begin
    if(!rst_n)
        dig<=6'b111_110;
    else
        dig<={dig[4:0],dig[5]};
end

//choose a num
reg [3:0] num;
always@(*) begin

```

```

    if(!rst_n)
        num = 4'hA;
    else begin
        case(dig)
            6'b111_110 : num = num_1;
            6'b111_101 : num = num_2;
            6'b111_011 : num = num_3;
            6'b110_111 : num = num_4;
            6'b101_111 : num = num_5;
            6'b011_111 : num = num_6;
            default : num = 4'hA;    //(A~F means seg off)
        endcase
    end
end

//dig output(A~F means seg off)
always@(*)
    case(num)
        4'h0 : seg = 7'h3f;
        4'h1 : seg = 7'h06;
        4'h2 : seg = 7'h5b;
        4'h3 : seg = 7'h4f;
        4'h4 : seg = 7'h66;
        4'h5 : seg = 7'h6d;
        4'h6 : seg = 7'h7d;
        4'h7 : seg = 7'h07;
        4'h8 : seg = 7'h7f;
        4'h9 : seg = 7'h6f;
        default : seg = 7'h00;
    endcase

endmodule

```

clock_division.v

```

module clock_division
    #(parameter DIVCLK_CNTMAX = 24999)
    (clk_in,rst_n,divclk);
    input  clk_in;
    input  rst_n;
    output reg divclk;

    reg [31:0] cnt;

```

```

always@(posedge clk_in, negedge rst_n) begin
    if(~rst_n) begin
        cnt<=0;
        divclk<=0;
    end
    else if(cnt == DIVCLK_CNTMAX) begin
        cnt <= 0;
        divclk <= ~divclk;
    end
    else
        cnt <= cnt + 1;
end

endmodule

```

bin2bcd.v

```

module bin2bcd (
    input  [5:0] bin,
    output [3:0] bcd_1,bcd_2
);
    integer i;
    reg [7:0] bcd_tmp;
    reg [5:0] bin_reg;
    always @(*) begin
        bin_reg=bin;
        bcd_tmp=0;
        repeat(6) begin
            if(bcd_tmp[3:0]>=5)
                bcd_tmp=bcd_tmp+3;
            if(bcd_tmp[7:4]>=5)
                bcd_tmp=bcd_tmp+(3<<4);
            bcd_tmp={bcd_tmp[6:0],bin_reg[5]};
            bin_reg=bin_reg<<1;
        end
    end

    assign bcd_1=bcd_tmp[3:0];
    assign bcd_2=bcd_tmp[7:4];

endmodule

```

Testbench code

```
`timescale 1ms/100us

module test;
    reg CLK1K;
    reg nRST;
    wire [6:0] seg;
    wire [5:0] dig;
    wire [7:0] led;


    traffic_light traffic_light(
        .CLK1K(CLK1K),
        .nRST(nRST),
        .seg(seg),
        .dig(dig),
        .led(led)
    );

    initial begin
        CLK1K=0;
        nRST=0;
        #20 nRST=1;
        forever
            #0.5 CLK1K=~CLK1K;
    end

    always begin
        #1000;
        if($time>=1000*100)
            $finish;
    end

endmodule
```

Simulation waveform

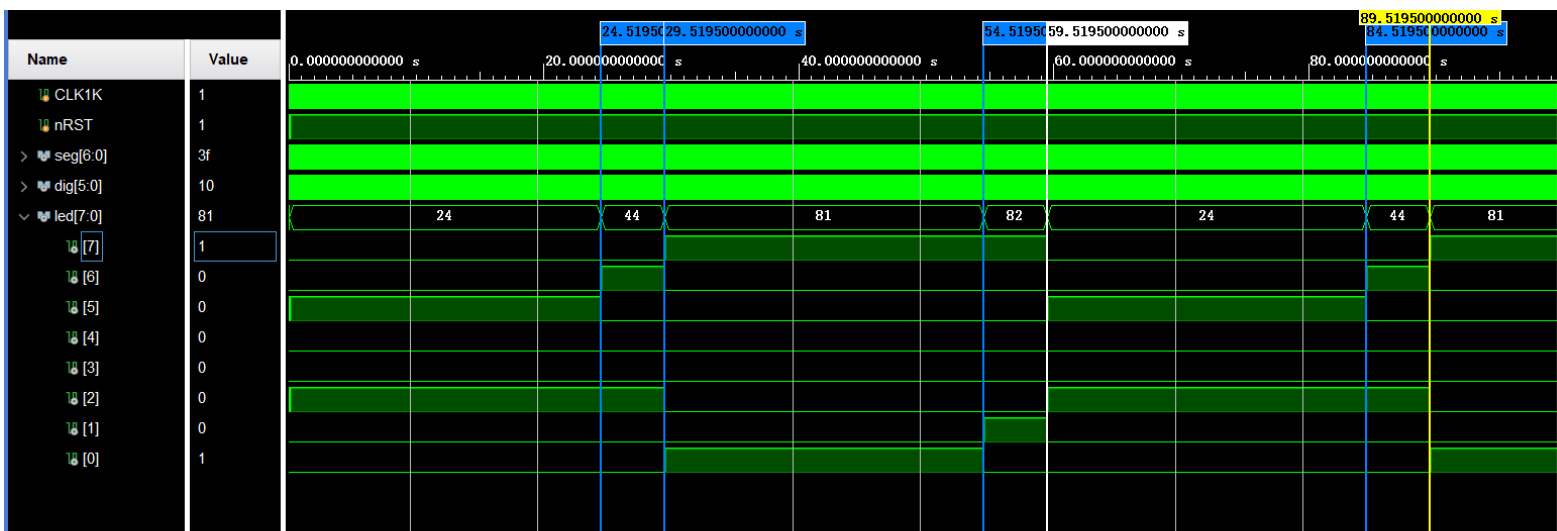

led[7:5]表示 B 通道的红灯、黄灯、绿灯

led[2:0]表示 A 通道的红灯、黄灯、绿灯

有下板测试

LED-T2~T4:左侧是 A 通道，LED-R7~R9:右侧是 B 通道